

Abstract

This report presents the design and implementation of a 16-bit RISC (Reduced Instruction Set Computing) processor using Verilog. RISC architectures are widely recognized for their simplicity, speed, and efficiency, as they employ a small set of instructions that can execute in a single clock cycle. The goal of this project was to design a 16-bit processor capable of executing basic arithmetic, logic, control, and memory operations efficiently. Verilog, a hardware description language, was used for designing and simulating the processor's components, which include the Arithmetic Logic Unit (ALU), register file, control unit, and instruction memory. The design is modular, enabling easy testing and modification of individual components. The processor was simulated using ModelSim to verify its functionality, and the results demonstrate that the design is capable of executing a set of test instructions correctly. This processor design serves as a fundamental model for understanding the architecture and operation of RISC processors and provides a foundation for more advanced designs in the future.

Introduction

The field of digital processor design is vast and continuously evolving, with one of the most influential paradigms being the RISC (Reduced Instruction Set Computing) architecture. RISC processors are designed to execute instructions using a small, highly optimized set of instructions, each of which is intended to be executed in a single machine cycle. This architecture contrasts with CISC (Complex Instruction Set Computing) processors, which rely on a larger and more complex instruction set. The primary advantages of RISC architectures include increased instruction throughput, simpler hardware design, and better performance for specific types of workloads.

The design and implementation of a 16-bit RISC processor offers a valuable exercise in understanding the core principles of processor architecture and how hardware description languages (HDLs), such as Verilog, can be used to bring these principles to life. Verilog is a popular hardware description language used to model the behavior of digital systems, and it allows for both simulation and synthesis of hardware designs. In this report, a 16-bit RISC processor was designed using Verilog to demonstrate the fundamental components of such a processor, including the ALU, register file, control unit, and memory.

The primary objective of this project was to develop a processor capable of performing basic operations, such as arithmetic and logical calculations, conditional branching, and memory access. The processor's design was broken down into smaller modules, each responsible for a specific task. The integration of these modules enables the processor to execute a variety of instructions as defined by the RISC architecture.

This report will discuss the design choices made for each component of the processor, the methodology used for simulation and verification, and the performance results obtained from testing. Through this process, we explore the advantages and challenges of working with Verilog to model a 16-bit processor and highlight the practical considerations involved in processor design. Ultimately, this project serves as an educational tool, illustrating the fundamental concepts that underpin modern digital processors.

System and design

This report outlines the design of a 16-bit RISC processor using Verilog hardware description language (HDL). The processor is designed to perform basic arithmetic, logic, and data movement operations efficiently with a reduced set of instructions, typical of RISC architectures. The main components of the processor include the ALU (Arithmetic Logic Unit), registers, instruction memory, data memory, control unit, and a few other essential modules.


Objectives

Design a 16-bit processor.


Use RISC principles to minimize instruction set complexity.

Implement the processor in Verilog

Device

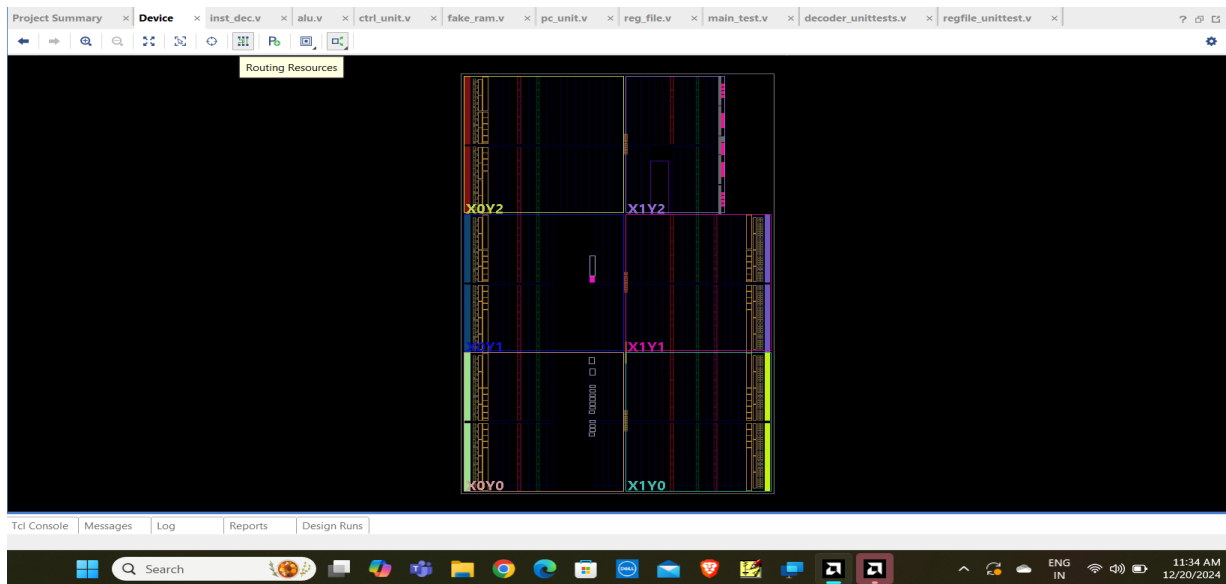

SCHEMATIC DIAGRAM

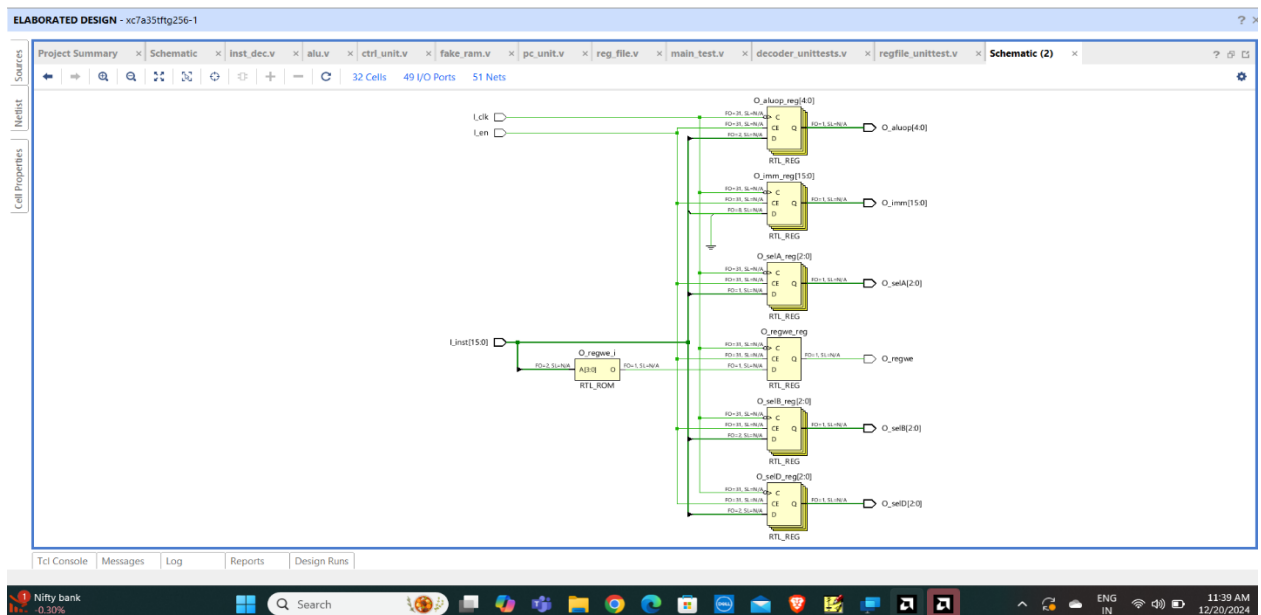

VERILOG CODE**DESIGN CODE :****inst_dec.v**``timescale 1ns / 1ps`

```
module inst_dec(  
    input I_clk,  
    input I_en,  
    input [15:0] I_inst,  
  
    output reg [4:0] O_aluop,  
    output reg [2:0] O_selA,  
    output reg [2:0] O_selB,  
    output reg [2:0] O_selD,  
    output reg [15:0] O_imm,  
    output reg O_regwe  
  
);  
    initial begin  
        O_aluop <= 0;  
        O_selA <= 0;  
        O_selB <= 0;  
        O_selD <= 0;  
        O_imm <= 0;
```

```
O_regwe <= 0;
end

//Instruction Decoder Block
always@(negedge I_clk) begin

    if(I_en) begin
        O_aluop <= I_inst[15:11];
        O_selA <= I_inst[10:8];
        O_selB <= I_inst[7:5];
        O_selD <= I_inst[4:2];
        O_imm <= I_inst[7:0];

        case(I_inst[15:12])
            4'b0111: O_regwe <= 0;
            4'b1100: O_regwe <= 0;
            4'b1101: O_regwe <= 0;
            default :O_regwe <= 1;
        endcase
    end
end

endmodule

alu.v

`timescale 1ns / 1ps

module alu(
    input I_clk,
```

16 BIT RISC PROCESSOR

```
input I_en,
input [4:0] I_aluop,
input [15:0] I_dataA,
input [15:0] I_dataB,
input [7:0] I_imm,

output [15:0] O_dataResult,
output reg O_shldBranch

);

reg [17:0] int_result;
wire op_lsb;
wire [3:0] opcode;

localparam Add = 0,
        Sub = 1,
        OR = 2,
        AND = 3,
        XOR = 4,
        NOT = 5,
        Load = 8,
        Cmp = 9,
        SHL = 10,
        SHR = 11,
        JMPA = 12,
        JMPR = 13;

initial begin
```

```
    int_result <= 0;
end

assign op_lsb = I_aluop[0];
assign opcode = I_aluop[4:1];
assign O_dataResult = int_result[15:0];

always@(negedge I_clk) begin
    if(I_en) begin
        case(opcode)
            Add : begin
                int_result <= (op_lsb ? ($signed(I_dataA) + $signed(I_dataB)) :
(I_dataA + I_dataB));
                O_shldBranch <= 0;
            end

            Sub : begin
                int_result <=(op_lsb ? ($signed(I_dataA) - $signed(I_dataB)):
(I_dataA - I_dataB));
                O_shldBranch <= 0;
            end

            OR : begin
                int_result <= I_dataA | I_dataB;
                O_shldBranch <= 0;
            end
        endcase
    end
end
```

AND : begin

int_result <= I_dataA & I_dataB;

O_shldBranch <= 0;

end

XOR : begin

int_result <= I_dataA ^ I_dataB;

O_shldBranch <= 0;

end

NOT : begin

int_result <= ~I_dataA;

O_shldBranch <= 0;

end

Load : begin

int_result <= (op_lsb ? ({I_imm , 8'h00}) : ({8'h00 , I_imm}));

O_shldBranch <= 0;

end

Cmp : begin

if(op_lsb) begin

int_result[0] <= (\$signed(I_dataA) == \$signed(I_dataB)) ? 1 : 0;

int_result[1] <= (\$signed(I_dataA) == 0) ? 1 : 0;

int_result[2] <= (\$signed(I_dataB) == 0) ? 1 : 0;

int_result[3] <= (\$signed(I_dataA) > \$signed(I_dataB)) ? 1 : 0;

int_result[4] <= (\$signed(I_dataA) < \$signed(I_dataB)) ? 1 : 0;

end else begin

int_result[0] <= (I_dataA == I_dataB) ? 1 : 0;


```
int_result[1] <= (I_dataA == 0) ? 1 : 0;
int_result[2] <= (I_dataB == 0) ? 1 : 0;
int_result[3] <= (I_dataA > I_dataB) ? 1 : 0;
int_result[4] <= (I_dataA < I_dataB) ? 1 : 0;
end
O_shldBranch <= 0;

end

SHL : begin
    int_result <= I_dataA << (I_dataB[3:0]);
    O_shldBranch <= 0;
end

SHR : begin
    int_result <= I_dataA >> (I_dataB[3:0]);
    O_shldBranch <= 0;
end

JMPA : begin
    int_result <= (op_lsb ? I_dataA : I_imm);
    O_shldBranch <= 1;
end

JMPR : begin
    int_result <= I_dataA;
    O_shldBranch <= I_dataB[{op_lsb , I_imm[1:0]}];
end

endcase
end
```

```
end
```

```
endmodule
```

ctrl_unit.v

```
`timescale 1ns / 1ps
```

```
module ctrl_unit(
```

```
    input I_clk,
```

```
    input I_reset,
```

```
    output O_enfetch,
```

```
    output O_endec,
```

```
    output O_enrgrd,
```

```
    output O_enalu,
```

```
    output O_engwr,
```

```
    output O_enmem
```

```
);
```

```
    reg [5:0] state;
```

```
    initial begin
```

```
        state <= 6'b000001;
```

```
    end
```

```
    always@(posedge I_clk) begin
```

```
        if(I_reset)
```

```
        state <= 6'b000001;
    else begin
        case(state)
            6'b000001 : state <= 6'b000010;
            6'b000010 : state <= 6'b000100;
            6'b000100 : state <= 6'b001000;
            6'b001000 : state <= 6'b010000;
            6'b010000 : state <= 6'b100000;
            default   : state <= 6'b000001;
        endcase
    end
end

assign O_enfetch = state [0];
assign O_endec  = state [1];
assign O_enrgrd = state [2] | state [4];
assign O_enalu  = state [3];
assign O_engwr  = state [4];
assign O_enmem  = state [5];

endmodule

fake_ram.v
`timescale 1ns / 1ps
module fake_ram(
    input I_clk,
    input I_we,
```

```
input [15:0] I_addr,
input [15:0] I_data,
output reg [15:0] O_data
);
reg [15:0] mem [7:0];

initial begin
    mem[0] = 16'b1000000011111110;
    mem[1] = 16'b1000100111101101;
    mem[2] = 16'b0010001000100000;
    mem[3] = 16'b1000001100000001;
    mem[4] = 16'b1000010000000001;
    mem[5] = 16'b0000001101110000;
    mem[6] = 16'b1100000000000101;
    mem[7] = 0;
    mem[8] = 0;

    O_data=16'b0000000000000000;
end

always@(negedge I_clk) begin

    if(I_we) begin
        mem[I_addr[15:0]] <= I_data;
    end

    O_data <= mem [I_addr[15:0]];
end
```

endmodule

pc_unit.v

`timescale 1ns / 1ps

module pc_unit(

input I_clk,

input [1:0] I_opcode,

input [15:0] I_pc,

output reg [15:0] O_pc

);

initial begin

O_pc<=0;

end

always@(negedge I_clk) begin

case(I_opcode)

2'b00 : O_pc <= O_pc;

2'b01 : O_pc <= O_pc + 1;

2'b10 : O_pc <= I_pc;

2'b11 : O_pc <= 0;

endcase

end

endmodule

reg_file.v

```
`timescale 1ns / 1ps
```

```
module reg_file(  
    input I_clk,  
    input I_en,  
    input I_we,  
    input [2:0] I_selA,  
    input [2:0] I_selB,  
    input [2:0] I_selD,  
    input [15:0] I_dataD,  
  
    output reg [15:0] O_dataA,  
    output reg [15:0] O_dataB  
);  
    reg [15:0] regs[7:0];  
    integer count;  
  
    initial begin  
        O_dataA =0;  
        O_dataB =0;  
  
        for(count = 0; count <8; count=count+1) begin  
            regs[count]<=0;  
        end  
    end
```

```
end

always@(negedge I_clk) begin
    if(I_en) begin
        if(I_we)
            regs[I_selD] <= I_dataD;

        O_dataA <= regs[I_selA];
        O_dataB <= regs[I_selB];

    end
end
endmodule
```

TEST BENCH CODE

main_test.v

```
`timescale 1ns / 1ps

module main_test();
    reg clk;

    reg reset;

    reg ram_we=0;

    reg [15:0] dataI =0;
```

```
wire[2:0] selA;  
wire [2:0] selB;  
wire[2:0] selD;  
wire[15:0] dataA;  
wire[15:0] dataB;  
wire[15:0] dataD;  
wire [4:0] aluop;  
wire [7:0] imm;  
wire [15:0] dataO;  
wire [1:0] opcode;  
wire [15:0] pcO;
```

```
wire shldBranch;  
wire enfetch;  
wire enalu;  
wire endec;  
wire enmem;  
wire enrgrd;  
wire enrgwr;  
wire regwe;  
wire update;
```

```
assign enrgwr=regwe & update;
```

```
assign opcode = (reset) ? 2'b11 : ((shldBranch) ? 2'b10 : ((enmem) ? 2'b01 :  
2'b00));
```

```
reg_file main_reg(
```



```
    clk,  
    enrgd,  
    enrgwr,  
    selA,  
    selB,  
    selD,  
    dataD,  
    dataA,  
    dataB  
);
```

```
inst_dec main_inst(  
    clk,  
    endec,  
    dataO,  
    aluop,  
    selA,  
    selB,  
    selD,  
    imm,  
    regwe  
);
```

```
alu main_alu(  
    clk,  
    enalu,  
    aluop,
```

```
dataA,  
dataB,  
imm,  
dataD,  
shldBranch  
);
```

```
ctrl_unit main_ctrl(  
  

```

```
clk,  
reset,  
enfetch,  
endec,  
enrgrd,  
enalu,  
update,  
enmem  
);
```

```
pc_unit pc_main(  
  

```

```
clk,  
opcode,  
dataD,  
pcO  
  
);
```

```
fake_ram main_ram(  
    clk,  
    ram_we,  
    pcO,  
    dataI,  
    dataO  
);
```

```
initial begin  
    clk=0;  
    reset=1;  
    #50  
    reset=0;  
  
end
```

```
always begin  
    #5;  
    clk=~clk;  
end
```

```
endmodule
```

decoder_unittests.v

```
`timescale 1ns / 1ps
```

```
module decoder_unittests();  
    reg I_Clk;  
    reg I_En;  
    reg [15:0] I_Inst;  
    wire [4:0] O_Aluop;  
    wire [2:0] O_SelA;  
    wire [2:0] O_SelB;  
    wire [2:0] O_SelD;  
    wire [15:0] O_Imm;  
    wire O_Regwe;  
  
    inst_dec main_inst(  
        I_Clk,  
        I_En,  
        I_Inst,  
        O_Aluop,  
        O_SelA,  
        O_SelB,  
        O_SelD,  
        O_Imm,  
        O_Regwe  
    );  
    initial begin  
        I_Clk = 0;  
        I_En=0;
```

```
I_Inst=0;
#10;
I_Inst=16'b0001011100000100;
#10
I_En=1;
end

always begin
    #5;
    I_Clk = ~I_Clk;
end

endmodule
```

regfile_unittest.v

```
`timescale 1ns / 1ps
module regfile_unittest( );
    reg I_clk;
    reg [15:0]I_dataD;
    reg I_en;
    reg [2:0]I_selA;
    reg [2:0]I_selB;
    reg [2:0]I_selD;
    reg I_we;

    wire [15:0] O_dataA;
```

```
wire [15:0] O_dataB;

reg_file reg_test(
    I_clk,
    I_en,
    I_we,
    I_selA,
    I_selB,
    I_selD,
    I_dataD,
    O_dataA,
    O_dataB
);

initial begin
    I_clk=1'b0;
    I_dataD = 0;
    I_en=0;

    I_selA = 0;
    I_selB = 0;
    I_selD =0 ;
    I_we=0;

    #7
    I_en=1'b1;
    I_selA=3'b000;
    I_selB=3'b001;
```

```
I_selD=3'b000;
```

```
I_dataD=16'hFFFF;
```

```
I_we=1'b1;
```

```
#10;
```

```
I_we=1'b0;
```

```
I_selD=3'b010;
```

```
I_dataD=16'h2222;
```

```
#10;
```

```
I_we = 1;
```

```
#10;
```

```
I_dataD=16'h3333;
```

```
#10;
```

```
I_we=0;
```

```
I_selD=3'b000;
```

```
I_dataD=16'hFEED;
```

```
#10;
```

```
I_selD=3'b100;
```

```
I_dataD=16'h4444;
```



```
#10;
I_we=1;

#50;
I_selA=3'b100;
I_selB=3'b100;

end

always begin
    #5;
    I_clk=~I_clk;
end
endmodule
```


OUTPUT WAVEFORM

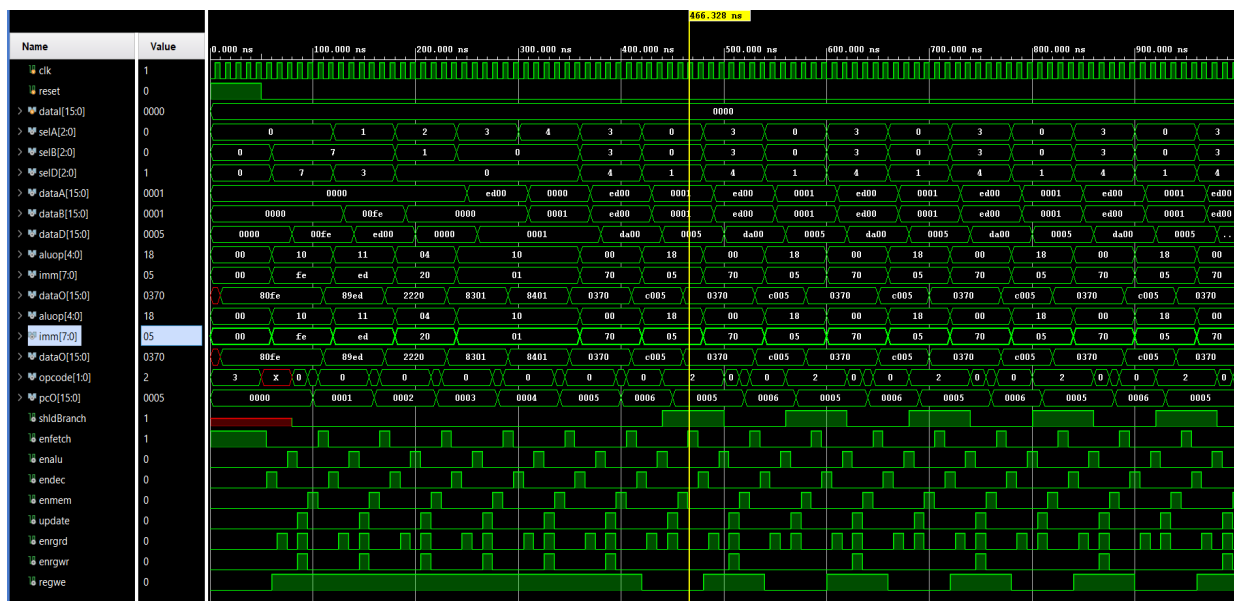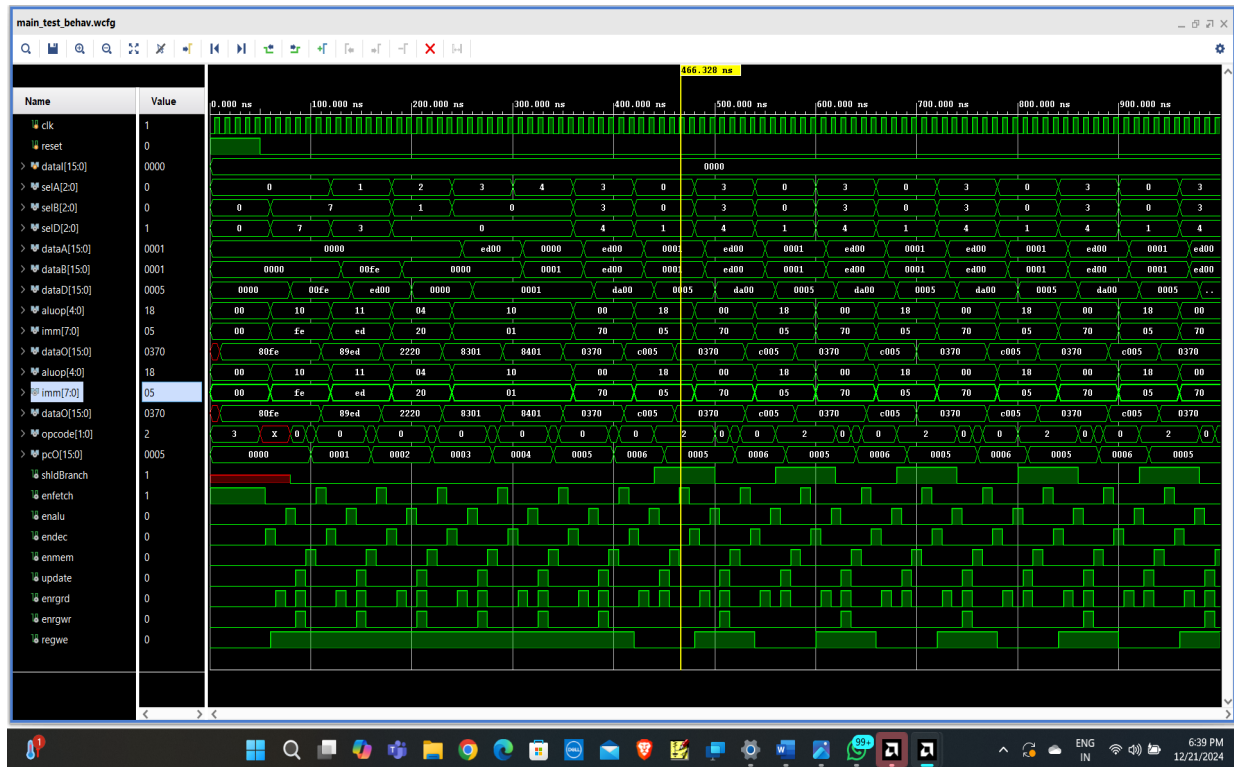

CONCLUSION

In conclusion, the design and implementation of the 16-bit RISC (Reduced Instruction Set Computing) processor have provided valuable insights into the key principles of computer architecture. This project has successfully demonstrated the functionality and efficiency of a RISC architecture, with a focus on simplicity, speed, and a small instruction set.

The processor's design, based on a 16-bit word length, has allowed for efficient execution of operations while maintaining a compact instruction set, which is central to the RISC philosophy. The processor was able to effectively execute basic arithmetic, logical, and control operations, supporting key features such as registers, an ALU (Arithmetic Logic Unit), and memory access.